

GreyHats - WelcomeCTF - EE2026 Reverse Engineering PoC

Open in vivado, open synthesis

Create Block Design

Open Block Design

Generate Block Design

▼ SIMULATION

Run Simulation

▼ RTL ANALYSIS

> Open Elaborated Design


▼ **SYNTHESIS**

▶ Run Synthesis

▼ **Open Synthesized Design**

Constraints Wizard


Edit Timing Constraints

 Set Up Debug

 Report Timing Summary

Report Clock Networks


Report Clock Interaction

 Report Methodology



Report DRC

Report Noise

Report Utilization

 Report Power

 [Schematic](#)

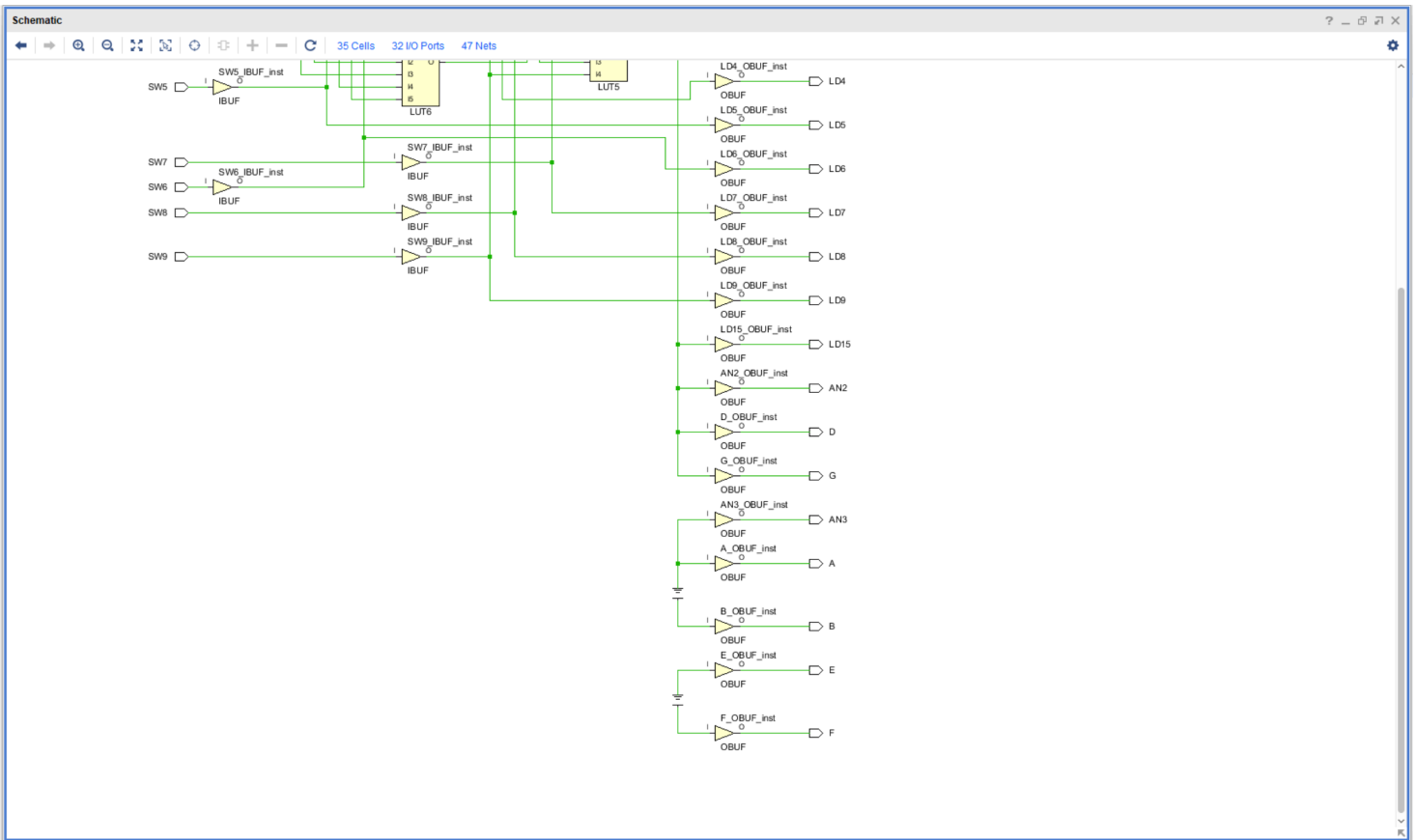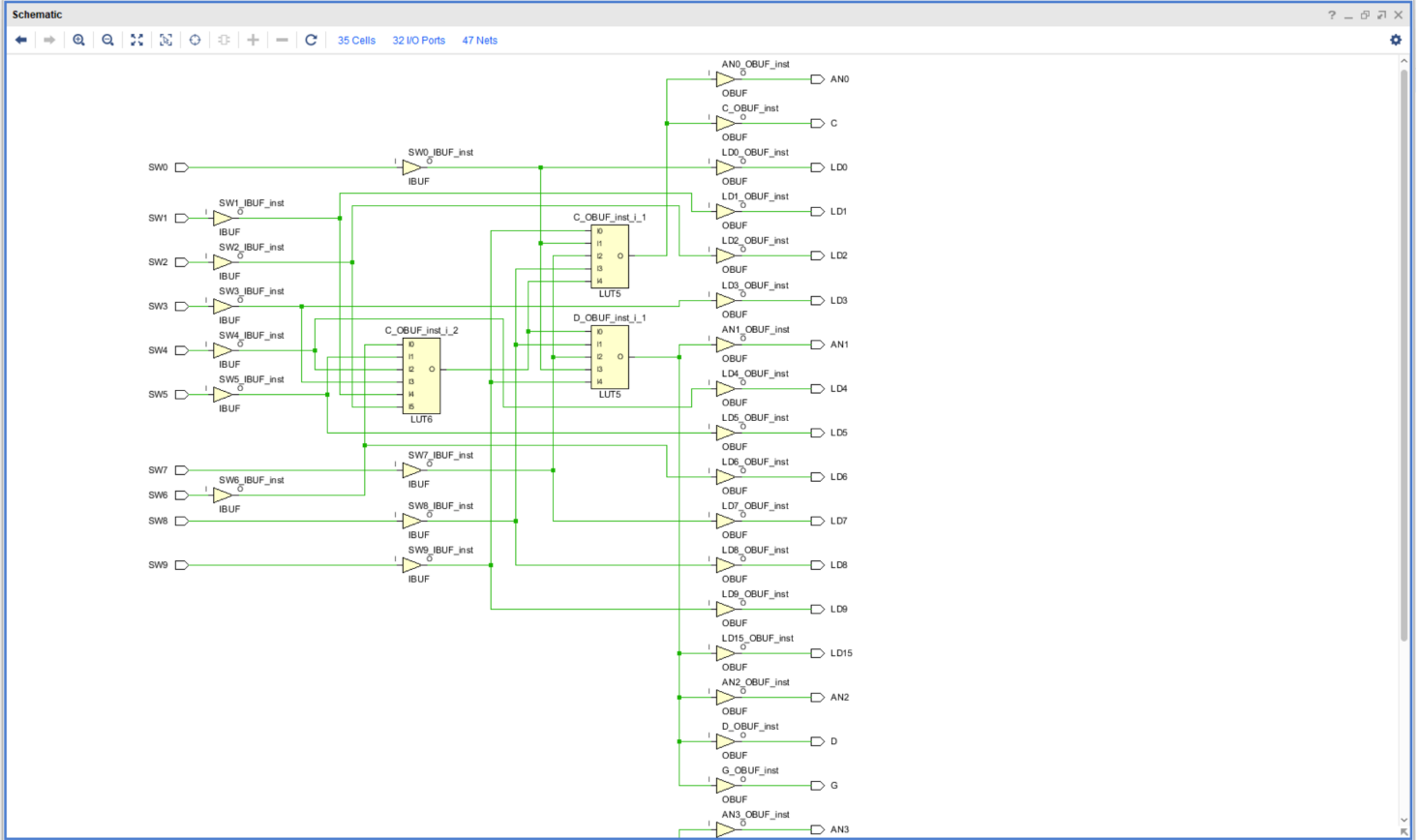

Subtask 2

LUT5

$0 = I0 \& I1 \& !I2 \& !I3 \& !I4$

$I0 = \text{LUT6}$

$I1 = \text{SW8}$

$I2 = \text{SW7}$

$I3 = \text{SW0}$

I4 = SW9

LUT6_0 & SW8 & !SW7 & !SW0 & !SW9

LUT6

0=!I0 & !I1 & I2 & !I3 & I4 & I5

I0 = SW6

I1 = SW5


I2 = SW4


I3 = SW3

I4 = SW1

I5 = SW2

!SW6 & !SW5 & SW4 & !SW3 & SW1 & SW2

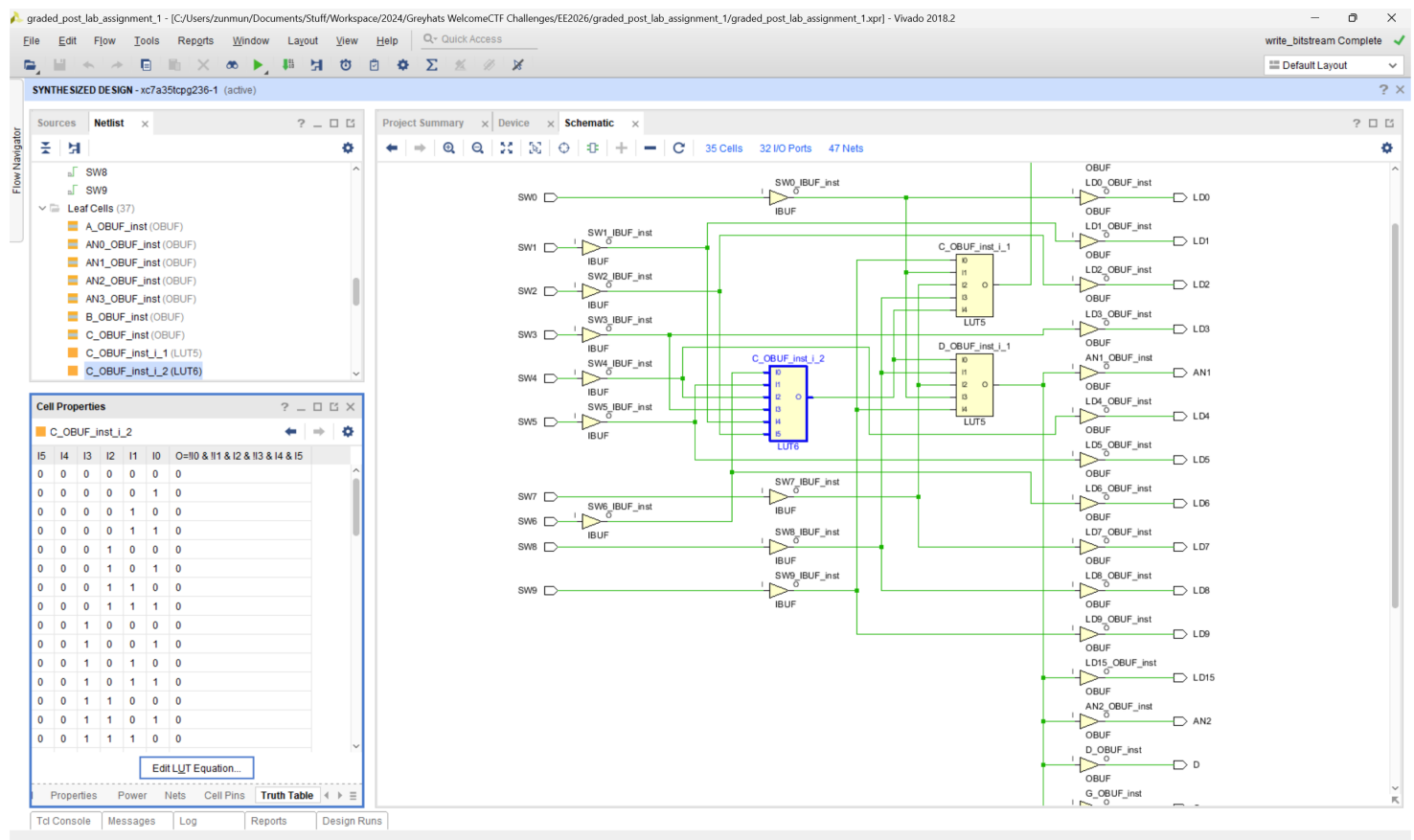

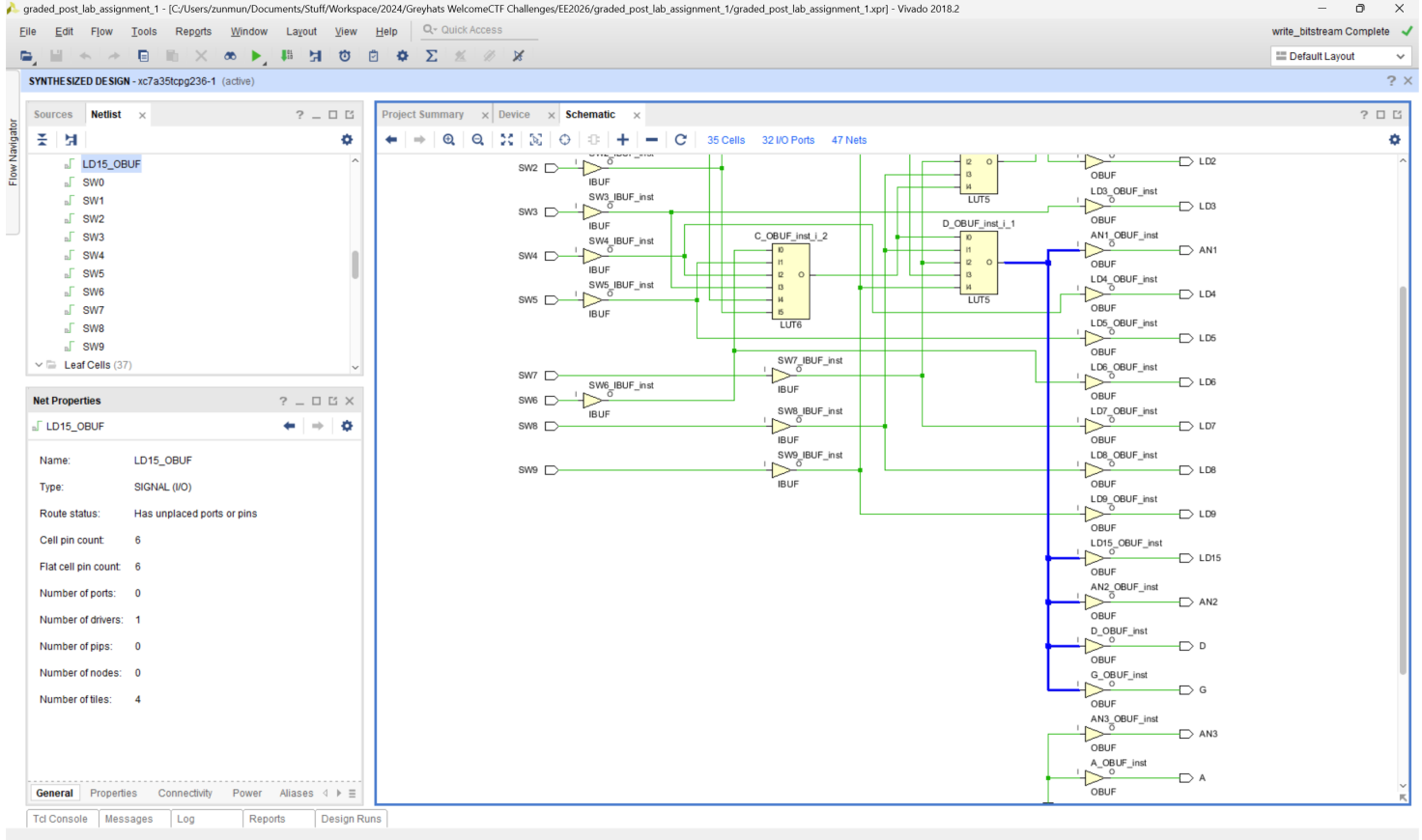


Final output


!SW6 & !SW5 & SW4 & !SW3 & SW1 & SW2 & SW8 & !SW7 & !SW0 & !SW9

Can rev the password to be

1248X

Subtask 3

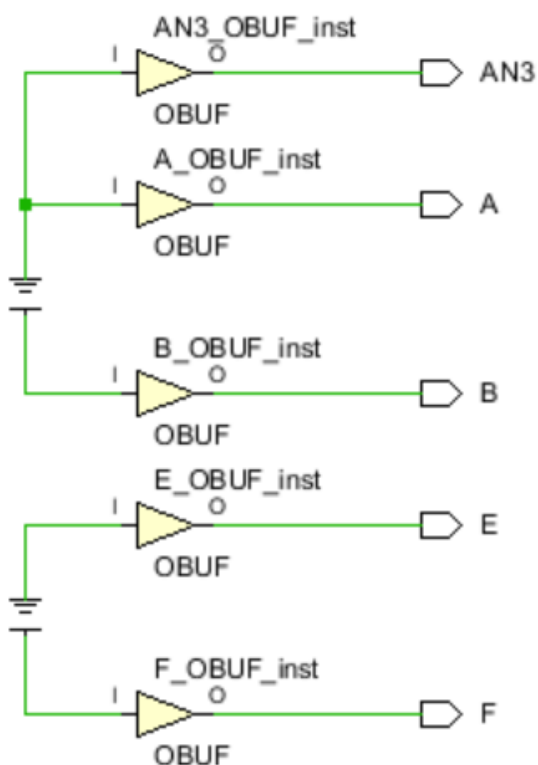

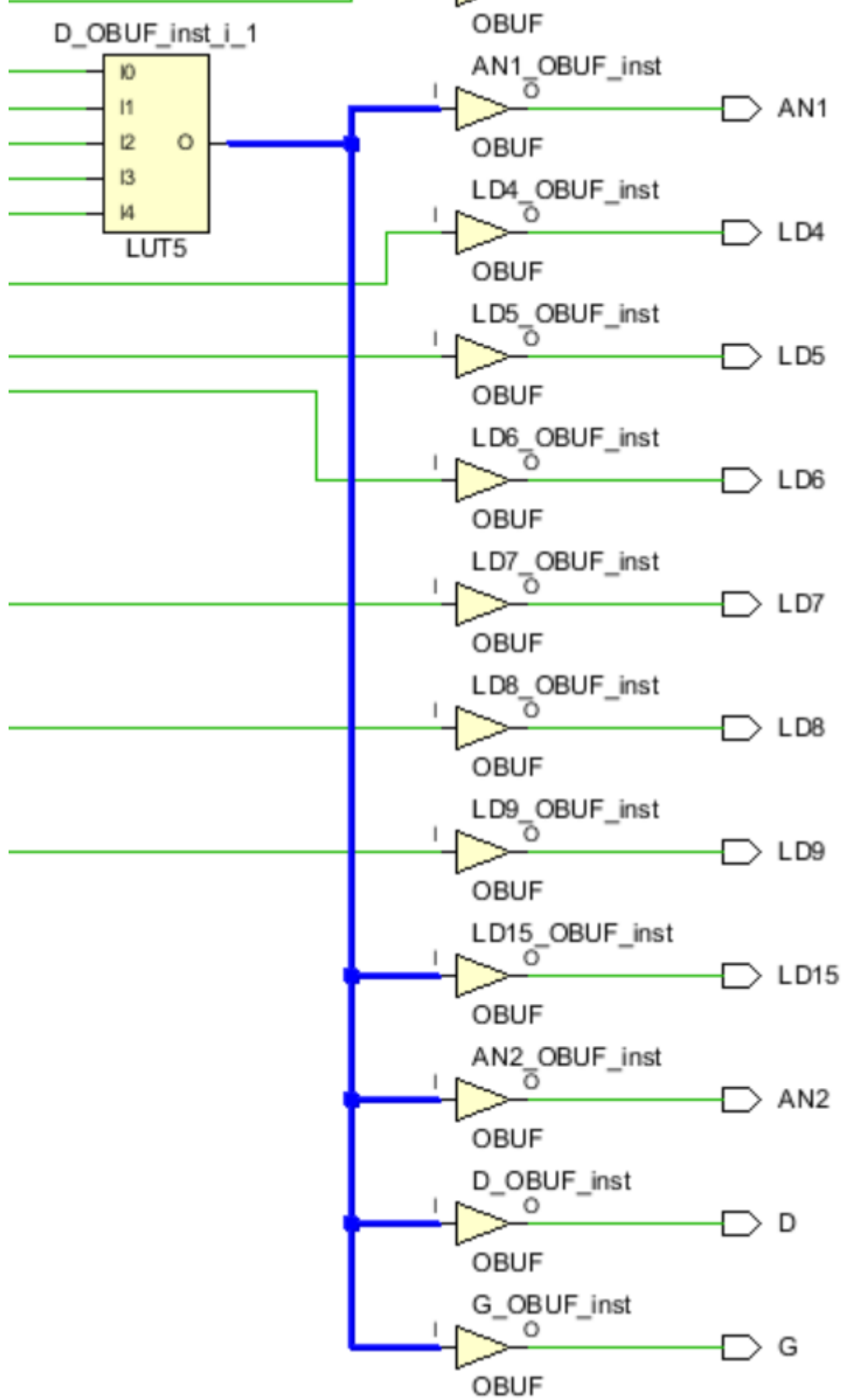


When switches are on

AN1=1

AN2=1

AN3=0

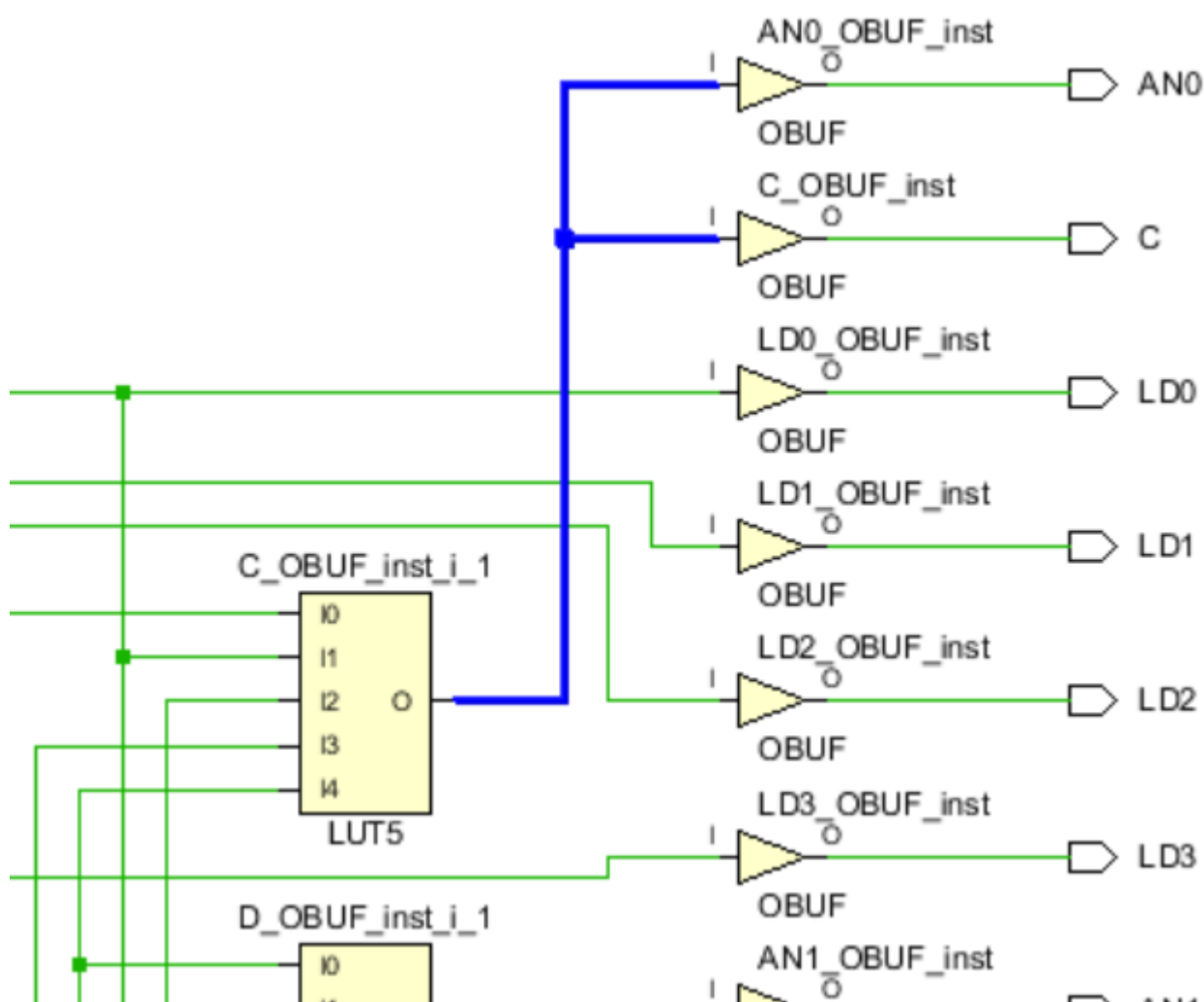

LUT5

$O = I0 + I1 + I2 + !I3 + !I4$

SW9

SW0

SW7

SW8

LUT6

$SW9 + SW0 + SW7 + !SW8 + !(SW6 + SW5 + !SW4 + SW3 + !SW1 + !SW2)$

$SW9 + SW0 + SW7 + !SW8 + (SW6 + SW5 + !SW4 + SW3 + !SW1 + !SW2)$

basically if password not pressed $\rightarrow AN0 = 1$

$AN0 = 0$

$AN1 = 1$

$AN2 = 1$

$AN3 = 0$

0110

but since active logic low (cathode) so its value

1001

ValueC = 8

Alphabet

AE=0
BF=1

C = 0 if LD15
DG = 1 if LD15

but because active logic low

 


Figure 18. Common anode circuit node.



Alphabet B maps over to G

Intro Subtask

When password not input

AN0=0 -> 1
AN1=1 -> 0
AN2=1 -> 0
AN3=0 -> 0

AE=0
BF=1


```
C = 0 if LD15 -> 1
DG = 1 if LD15 -> 0
```

```
active high, so maps to
ACE = 0
BDFG = 1
```

```
value A = 2
```

Final

```
grey{21248xG8}
```